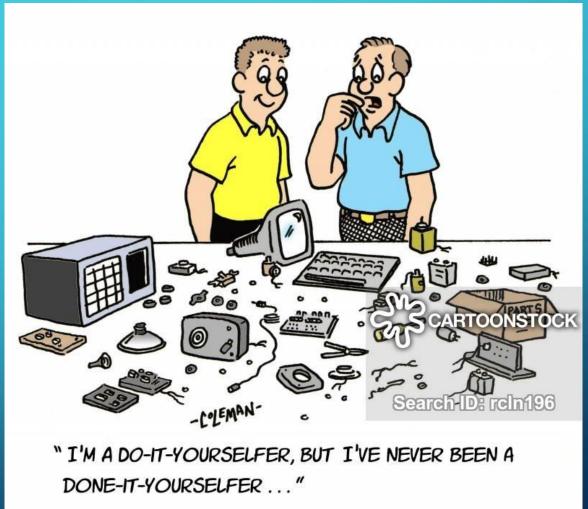




#### **AGENDA**

- Introduction
- Course overview
- What is electricity?
- Important terms and how they relate
- How to make your light shine







#### **WEEKLY FORMAT**

- Start 6pm
- Introduction and theory 20 30 mins
- Q & A 5 10 mins
- Practical demo 15 20 mins
- Work on projects 60 mins
- Finish 8pm



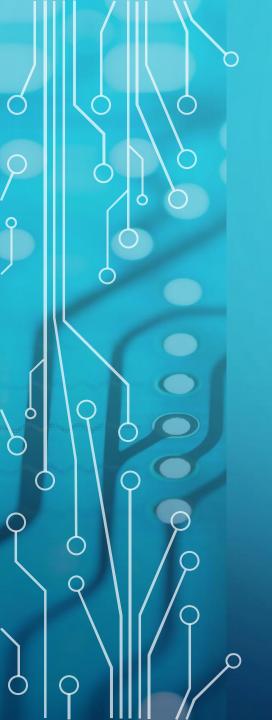
#### **COURSE CONTENTS**


- Week 1 (5/10/20) 3 ways to blink a light (H/W)
- Week 2 (12/10/20) 3 ways to blink a light (S/W)
- Week 3 (19/10/20) Resistors, capacitors and inductors (H/W)
- Week 4 (26/10/20) learning to count, again! (S/W)
- Week 5 (02/11/20) Diodes and transistors (H/W)
- Week 6 (09/11/20) loops and logic (S/W)
- Week 7 (16/11/20) AC/DC, time and frequency domains (H/W)
- Week 8 (23/11/20) functions and arguments (S/W)
- Week 9 (30/11/20) digital-to-analog and analog-to-digital converters (H/W)
- Week 10 (7/12/20) arrays and strings (S/W)
- Week 11 (14/12/20) motors and how to drive them (H/W)








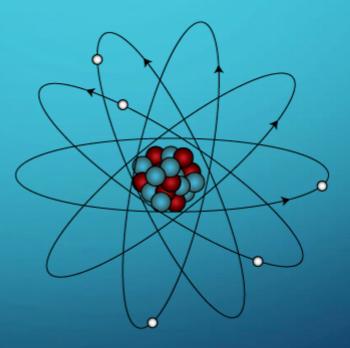Flow of charged particles called electrons



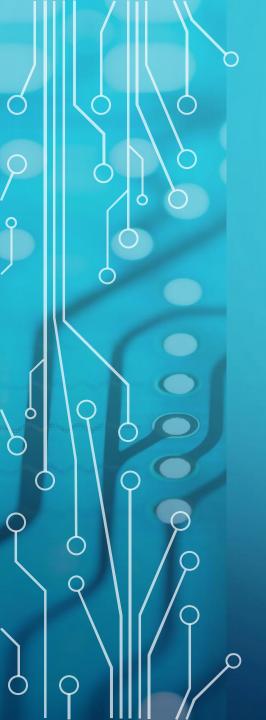

Flow of charged particles called electrons


 Measure of their potential energy is called voltage (Volts)




Flow of charged particles called electrons

 Measure of their potential energy is called voltage (Volts)


Rate of flow is called current (Amperes)

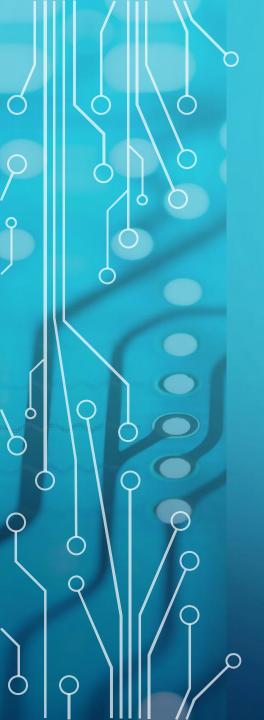

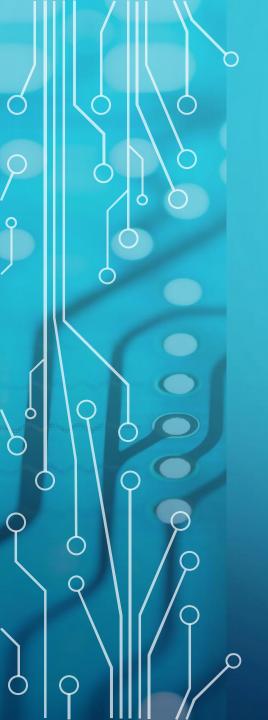 Current and voltage are related by a term called resistance (Ohms)


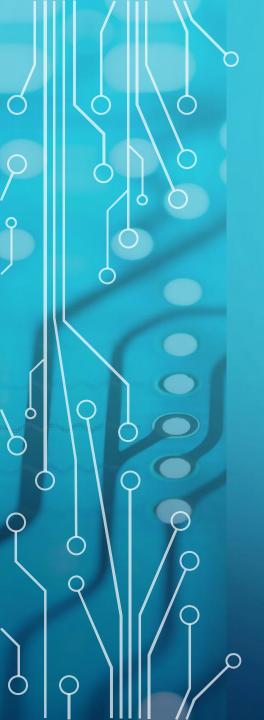
# MOST IMPORTANT EQUATION IN ELECTRONICS?




# MOST IMPORTANT EQUATION IN ELECTRONICS?

Voltage = Current x Resistance

Or

V = IR

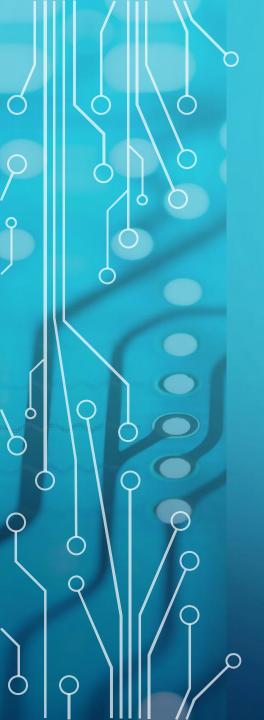

# A VISIBLE ANALOGY

Voltage: the height of the water tank





# A VISIBLE ANALOGY

Voltage: the height of the water tank



Current: the rate at which the water is released



### A VISIBLE ANALOGY

Voltage: the height of the water tank




Current: the rate at which the water is released


Resistance: the thickness of the water pipe





- A simple circuit using a:
  - Power source (+5V)
  - A Light Emitting Diode (LED)
  - A resistor

• How big should the resistor be?

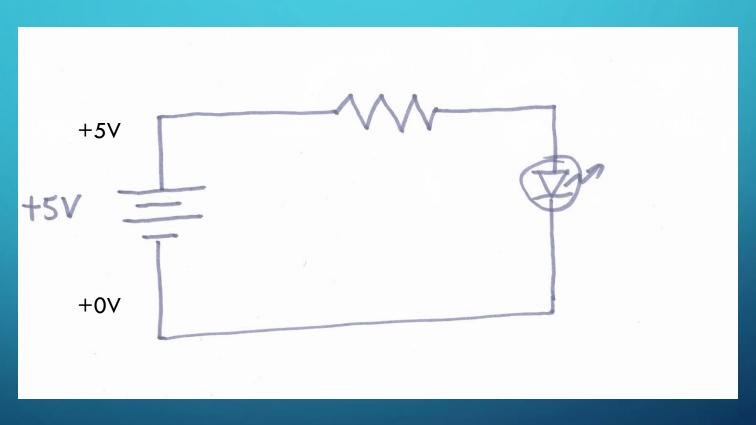

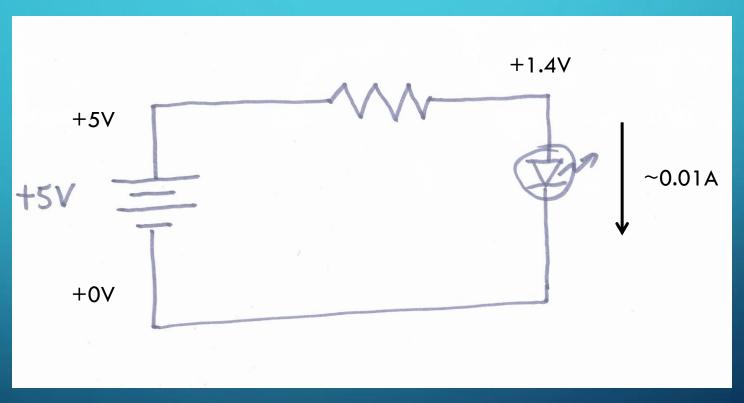

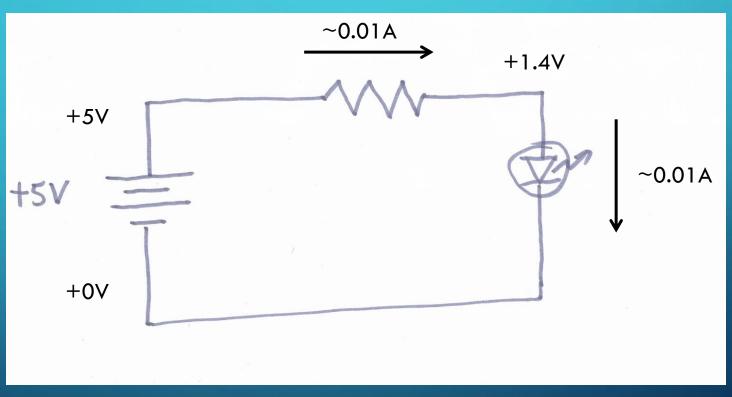

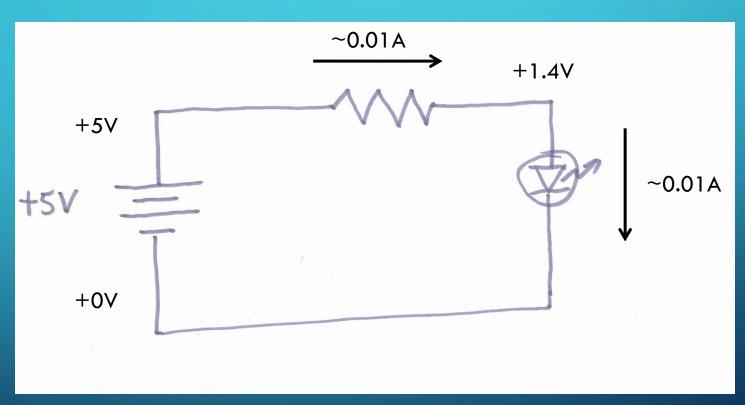

 $V = I \times R$ 

I: 0.01 A


V: 5 - 1.4 = 3.6V

 $B = \dot{s}$ 


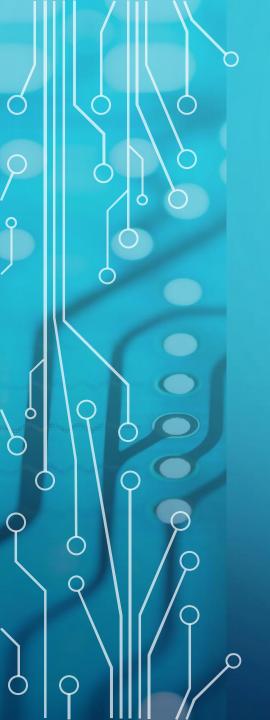
# MAKING OUR LIGHT BLINK

- •Introduce a switch
- Build an oscillator
- Multivibrator
- •555 Timer



# QUESTIONS