



WEEK 3: BASIC COMPONENTS

CENTENARY SUBURBS MEN'S SHED – ELECTRONICS GROUP



AGENDA

- Resistors
- Capacitors
- Inductors
- A simple capacitance meter using a Raspberry Pi

RESISTANCE





RESISTANCE

- What is resistance?

"A resistor is a passive two-terminal electrical component that implements electrical resistance as a circuit element." *Wikipedia*



RESISTANCE

- Useful for converting a current to a voltage and vice versa
- Used to limit current flow
- Useful for setting reference currents
- Adjust signal levels



RESISTANCE

Fixed:

“Fixed resistors have resistances that only change slightly with temperature, time or operating voltage.”



RESISTANCE

Fixed:

"Fixed resistors have resistances that only change slightly with temperature, time or operating voltage."

Variable:

"Variable resistors can be used to adjust circuit elements (such as a volume control or a lamp dimmer), or as sensing devices for heat, light, humidity, force, or chemical activity."



RESISTANCE

Remember Ohms law

$$V = I \times R$$



RESISTANCE

Second most important law

$$P = V \times I$$

Where P: power in Watts



RESISTANCE

Second most important law

$$P = V \times I$$

Where P: power in Watts

Therefore:

$$P = I \times R \times I$$

Or

$$= I^2 R$$



WARNING!

When using a resistor always make sure it's operating below it's rated power

WARNING!

When using a resistor always make sure it's operating below it's rated power



RESISTORS IN CIRCUITS

In series:



RESISTORS IN CIRCUITS

In series:




$$R1 = 1\text{k}\Omega$$

$$R2 = 4\text{k}\Omega$$

$$\begin{aligned} R_{\text{total}} &= R1 + R2 \\ &= 5\text{k}\Omega \end{aligned}$$


RESISTORS IN CIRCUITS

In parallel:

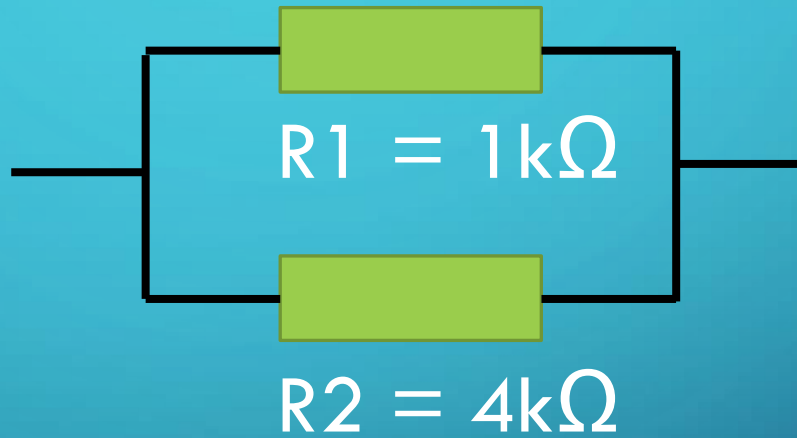

RESISTORS IN CIRCUITS

In parallel:

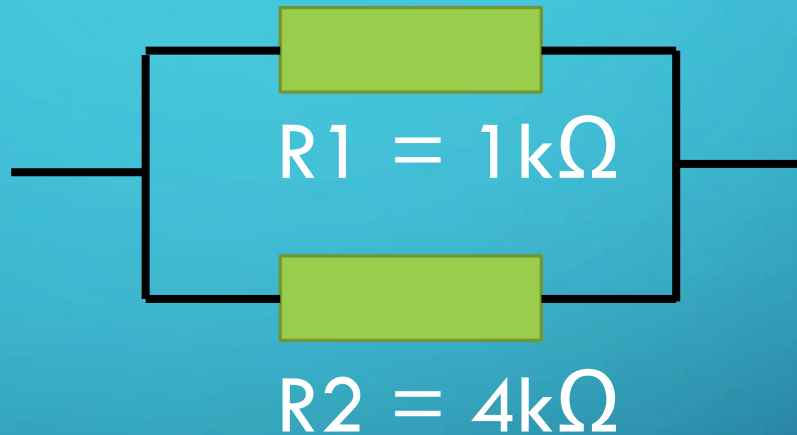

$$1/R_{\text{total}} = 1/R1 + 1/R2$$

$$R_{\text{total}} = (R1 \times R2) / (R1 + R2) \\ = 800 \Omega$$



THINGS TO REMEMBER!

Resistors:

- Calculate power dissipation and always make sure power rating of resistor is greater than this
- Use resistors in parallel or series to boost power handling

A collection of various electronic components, including capacitors and resistors, arranged on a light-colored surface. The components include: four electrolytic capacitors of different sizes and values (50V 100uF, 35V 470uF, 35V 470uF, 35V 470uF); two blue electrolytic capacitors (25V 3300uF, 25V 3300uF); a large blue electrolytic capacitor (25V 3300uF); several small surface-mount capacitors (15 16V, 33 16V); several small through-hole capacitors (15 16V, 33 16V); a small blue electrolytic capacitor (25V 3300uF); and a small blue electrolytic capacitor (25V 3300uF).

CAPACITORS



CAPACITORS



CAPACITORS



A decorative graphic on the left side of the slide, featuring a vertical strip of white circuit lines and nodes on a blue background.

CAPACITANCE: WHAT IS IT?


"Capacitance is the ratio of the change in electric charge of a system to the corresponding change in its electric potential." *Wikipedia*



CAPACITORS: WHY WE USE THEM?

- Local energy storage
- Blocking DC voltages
- Smoothing voltage ripple
- Suppressing noise and spikes
- Filtering or discriminating signals

CAPACITORS

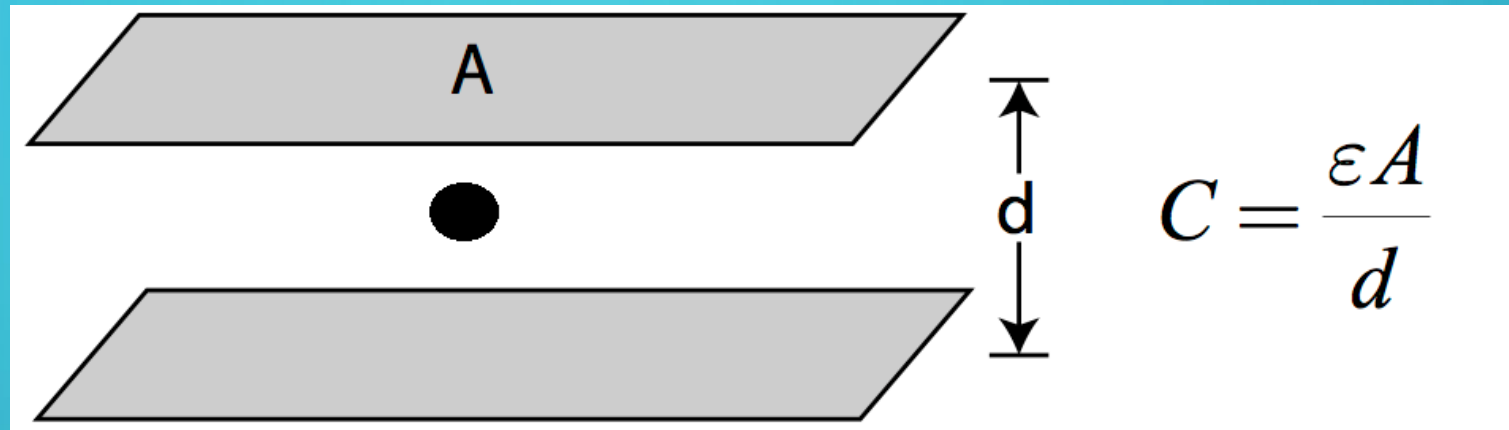

Capacitance of two parallel plates:

$$C = \epsilon_0 \times \epsilon_r \times A / d$$

Where A: area (m²)

d: distance between plates (m)

ϵ_0 : permittivity (8.854×10^{-12} C N / m²)

ϵ_r : relative permittivity (air = 1)

CAPACITORS

Capacitance of two parallel plates:

$$C = \epsilon_0 \times \epsilon_r \times A / d$$

Where A: area (m²)

d: distance between plates (m)

ϵ_0 : permittivity ($8.854 \times 10^{-12} \text{ C N} / \text{m}^2$)

ϵ_r : relative permittivity (air = 1)

We can use changes in capacitance to determine changes in moisture etc.



CAPACITANCE: WHAT IS IT?

How much electrical energy a component can store:

$$C = Q / \Delta V$$

where C : Farads
Q : Coulombs
V : Volts



CAPACITANCE: WHAT IS IT?

Since:

$$I = dQ / dt$$


Then:

$$I = C dV / dt$$

This means the voltage across the leads of a capacitor can't change instantaneously!


CAPACITORS WITH RESISTORS

Charging a capacitor:

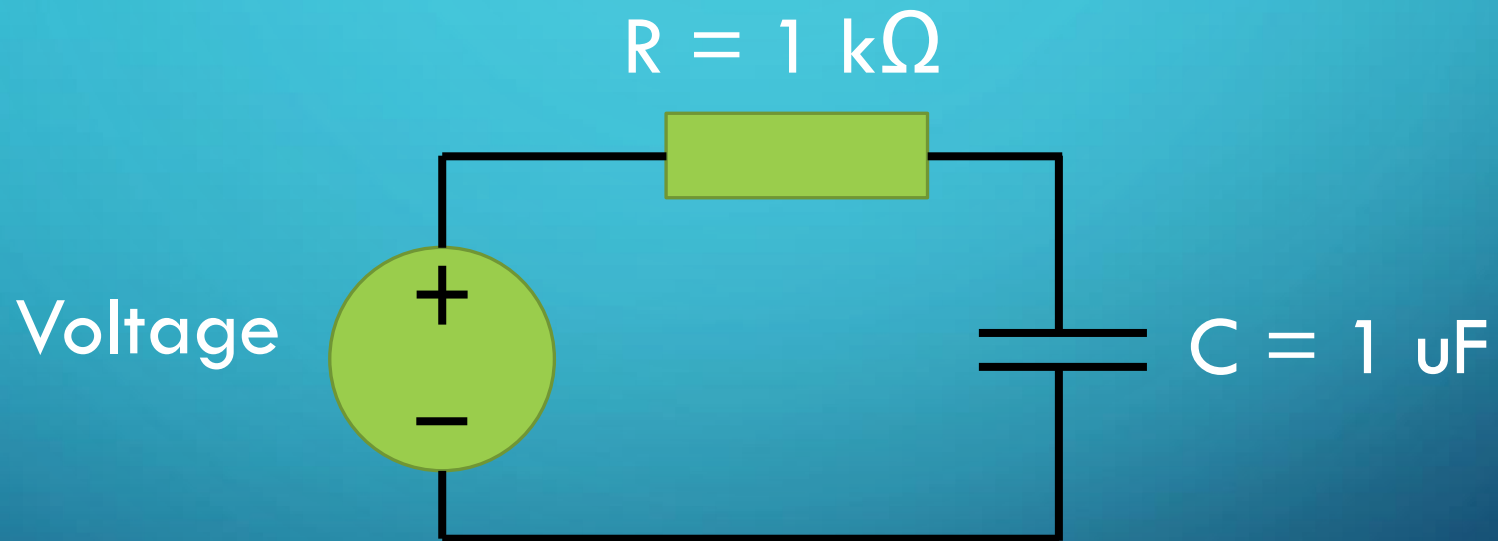

CAPACITORS WITH RESISTORS

Charging a capacitor:

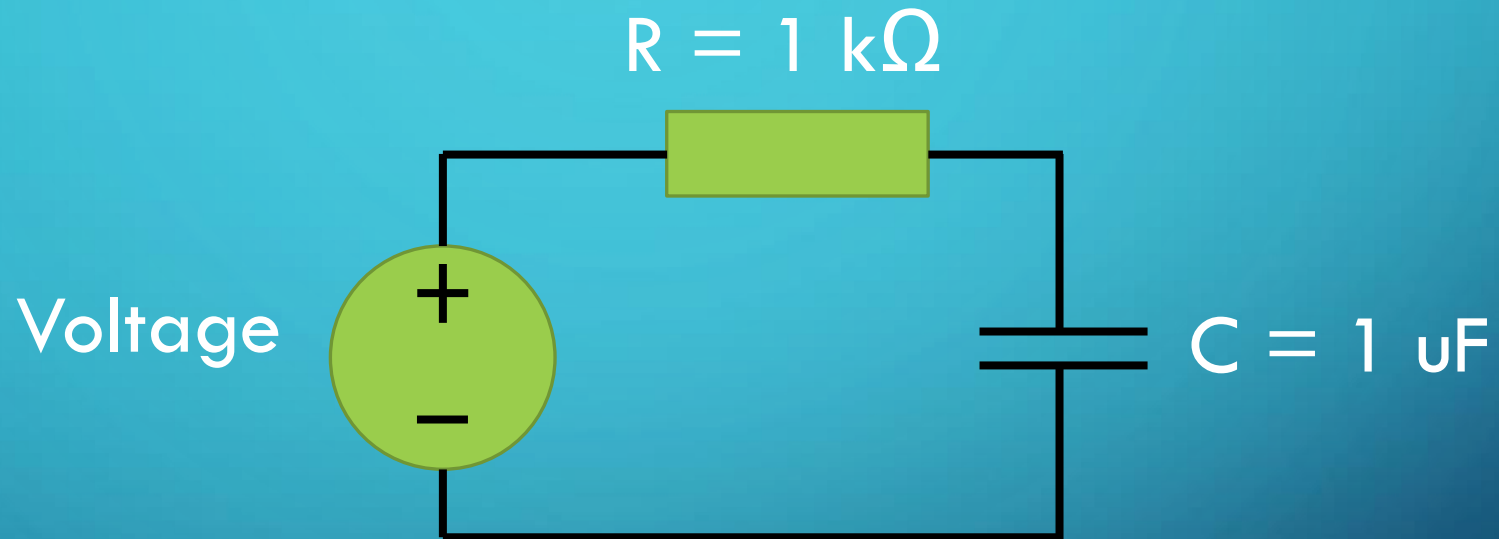

RC time constant (time for a capacitor to reach 2/3 of the charge voltage):

$$\tau = R \times C$$

CAPACITORS IN CIRCUITS

In series:



CAPACITORS IN CIRCUITS

In series:




$$1/C_{\text{total}} = 1/C1 + 1/C2$$

$$C_{\text{total}} = (C1 \times C2) / (C1 + C2) \\ = 0.8 \mu F$$

CAPACITORS IN CIRCUITS

In parallel:

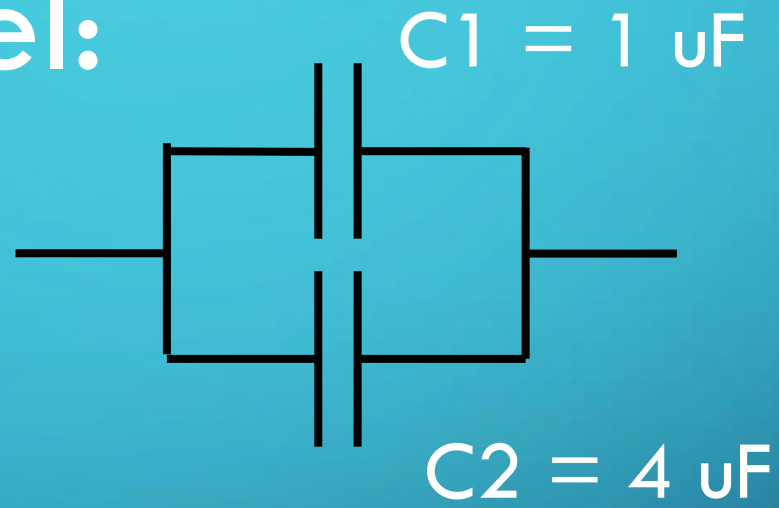

$$\begin{aligned} C_{\text{total}} &= C1 + C2 \\ &= 5 \mu\text{F} \end{aligned}$$



TYPES OF CAPACITORS

Electrolytic: Large values, large size, low cost,
unreliable at high temps, available at
high voltages, polarised

Tantalum: Medium values, medium size, mod cost
low to medium voltages, polarised

Ceramic: Small values, small size, low cost
low to medium voltages, *non*-polarised



THINGS TO REMEMBER!

Resistors:

- Calculate power dissipation and always make sure power rating of resistor is greater than this

Capacitors:

- Select capacitor based on required capacitance, size, characteristics and cost
- Make sure the operating voltage of the capacitor is always less than its rated voltage
- Ensure they have the right polarity

A decorative graphic on the left side of the slide, consisting of white lines and circles on a blue background, resembling a circuit board or a stylized tree structure.

QUESTIONS?



DEMO: BUILD A CAPACITANCE METER

- Measure the time it takes to charge a capacitor to $\frac{2}{3}$ its operating voltage



DEMO: BUILD A CAPACITANCE METER

- Measure the time it takes to charge a capacitor to $\frac{2}{3}$ its operating voltage
- Use this measured time constant and the known value of the resistor to calculate the capacitance




DEMO: BUILD A CAPACITANCE METER


Required:

- Capacitor to measure
- 4 resistors of the same value (ie. 10k)
- A comparator (eg. LM393)
- A pull-up resistor (1 to 10k)
- A Raspberry Pi


DEMO: BUILD A CAPACITANCE METER

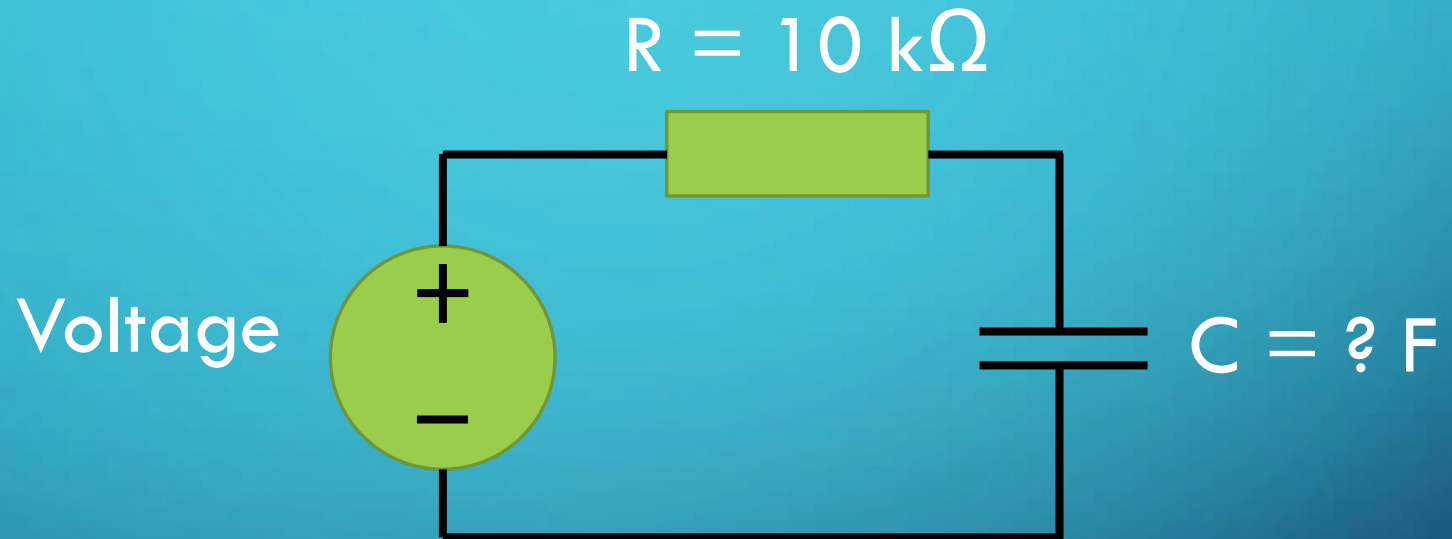

DEMO: BUILD A CAPACITANCE METER

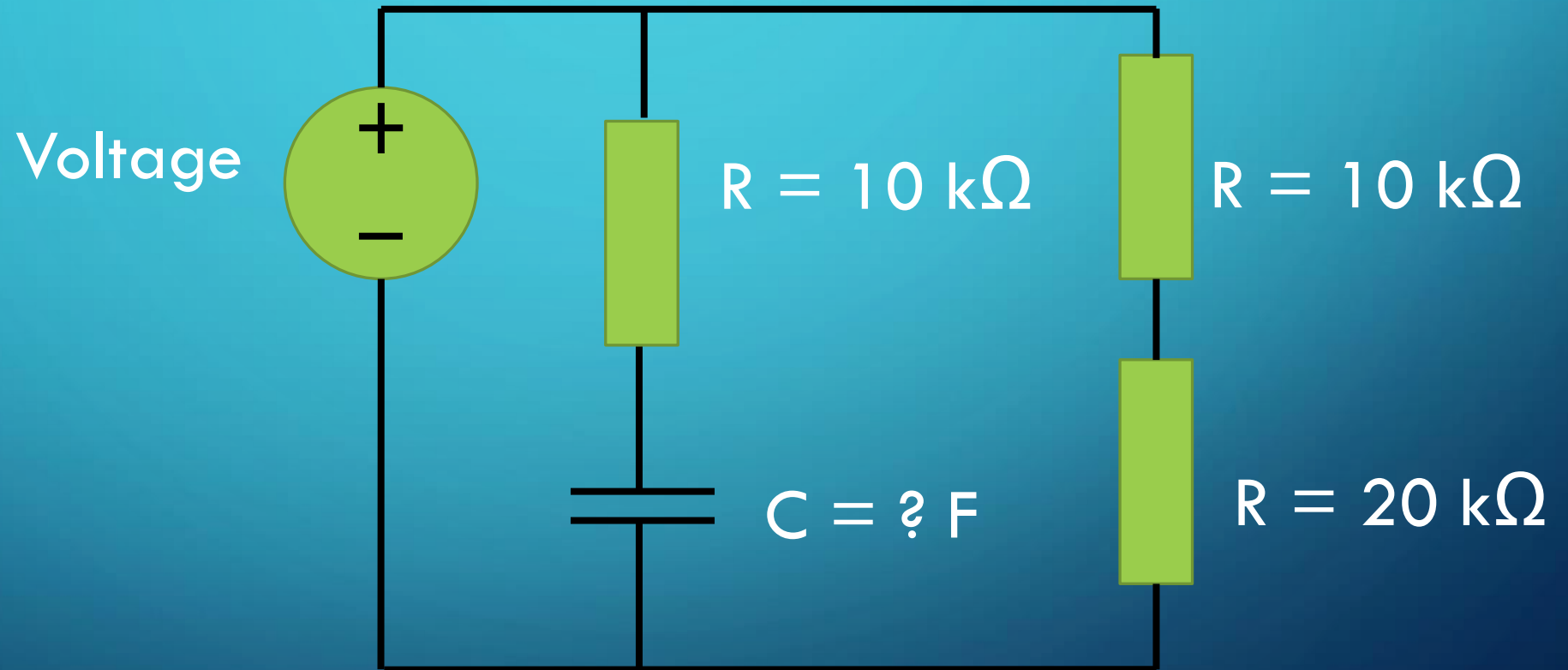

DEMO: BUILD A CAPACITANCE METER

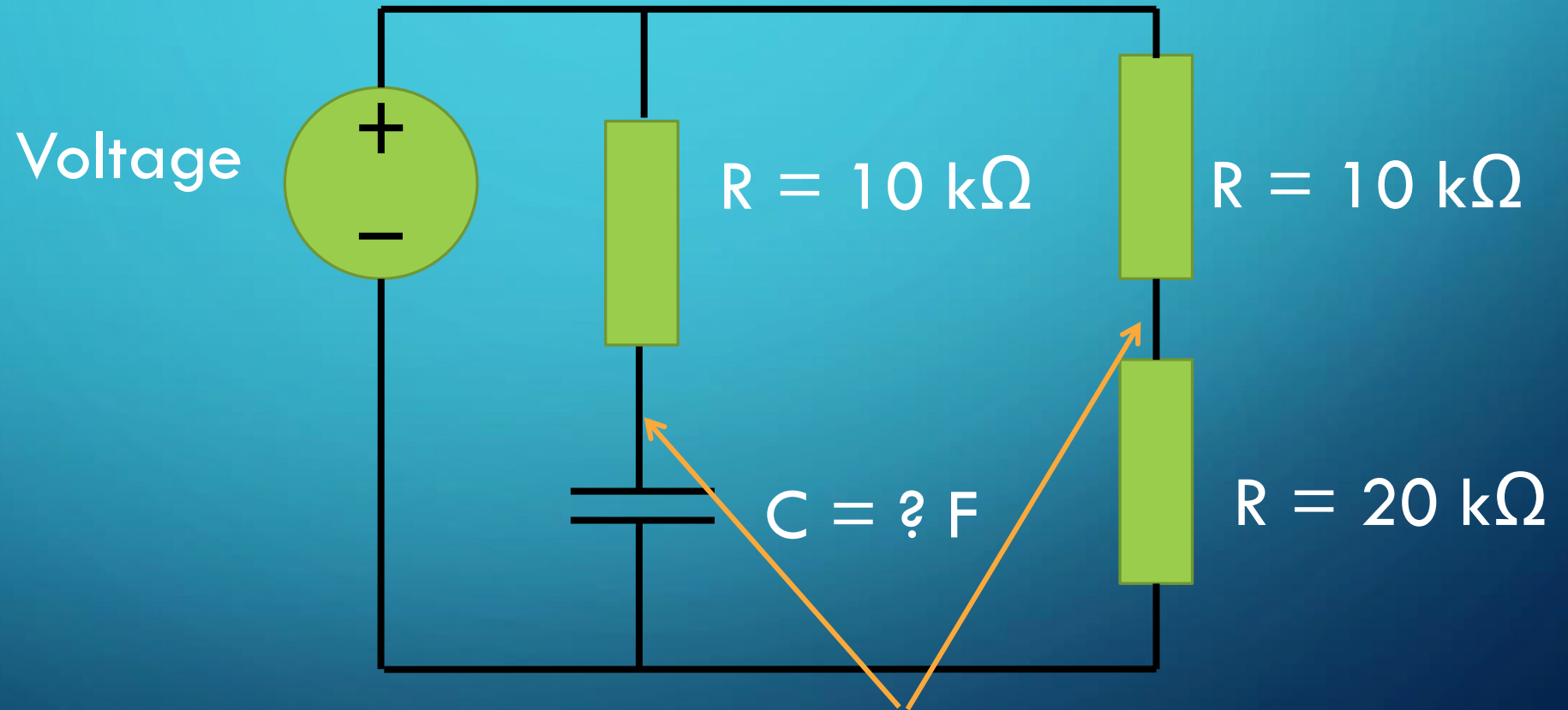

Compare these points

DEMO: BUILD A CAPACITANCE METER

